

National Cheng Kung University

Department of Electrical Engineering

Introduction to VLSI CAD

Lab Session 2

**Design and Simulation of K-map simplifier,
Multiplier and Ripple Carry Adder**

Objectives:

Help students get familiar with the CAD tools (NC-Verilog & Verdi) for digital logic design. Please go through the hands-on exercise step-by-step.

Prob A: Design Steps


1) Understand the K-map method and gate level.

Exercise 1-1: Simplifying the giving truth table using K-map method(Please describe/draw your procedure clearly). Draw a Schematic View of your simplified circuit (gate-level diagram)


A	B	C	D	Out
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

AB \ CD	00	01	11	10
00	0	1	1	0
01	1	1	0	1
11	1	1	1	1
10	0	1	1	0
 
$$\begin{aligned}
 \text{SOP} &= \bar{C}D + AB + BD + \bar{B}\bar{D} \\
 &= B(A + \bar{D}) + D(\bar{B} + C) \\
 &= (\bar{B} + A\bar{D})' + (D + B\bar{C})' \\
 &= (\bar{B} + (A + \bar{D}))' + (D + (B + C))'
 \end{aligned}$$



 2) Design your circuit(simplified by K-map method) with only NOR gate in it.



3) Implement your simplified circuit based on the gate-level diagram you drawn in 2) by verilog code. (The module name should be **kmap**)

➔ You only need to upload your v-code file to moodle, **do not** paste your code here.

4) Read the testbench for a kmap you implemented in 4). (The module is named **kmap_tb**)

➔ You only need to upload your v-code to moodle, **do not** paste your code here.

5) Compile the code you implemented in 4) using NC-Verilog. If there are errors, please go back to 3) to debug your code and re-compile again.

(Hint : The command for compiling is **%ncverilog kmap.v**)

6) Simulate your design in 3) with the testbench in 4).

(Hint: The command for simulation is

%ncverilog kmap_tb.v kmap.v +access+r +define+FSDB)


7) Verify your design by comparing the simulation results with the results you predicted. If the results are not the same, please go back to 3) and revise your code. If the simulation results are correct, please snapshot the simulation result on the terminal and the waveform you dumped and *explain your waveform*. (Hint : The command to open nWave is **%nWave &)**

In addition, you should check your coding style, there are no error messages and over 90% coverage with Superlint. Snapshot the result and *calculate Superlint coverage*. (Hint: The command to open Superlint is `%jg -superlint superlint.tcl`)

Your simulation result on the terminal.

```
Verdi* : End of traversing.
      0ns, A=0, B=0, C=0 , D=0 , Out=0
      10ns, A=0, B=0, C=0 , D=1 , Out=1
      20ns, A=0, B=0, C=1 , D=0 , Out=0
      30ns, A=0, B=0, C=1 , D=1 , Out=1
      40ns, A=0, B=1, C=0 , D=0 , Out=1
      50ns, A=0, B=1, C=0 , D=1 , Out=1
      60ns, A=0, B=1, C=1 , D=0 , Out=1
      70ns, A=0, B=1, C=1 , D=1 , Out=0
      80ns, A=1, B=0, C=0 , D=0 , Out=0
      90ns, A=1, B=0, C=0 , D=1 , Out=1
     100ns, A=1, B=0, C=1 , D=0 , Out=0
     110ns, A=1, B=0, C=1 , D=1 , Out=1
     120ns, A=1, B=1, C=0 , D=0 , Out=1
     130ns, A=1, B=1, C=0 , D=1 , Out=1
     140ns, A=1, B=1, C=1 , D=0 , Out=1
     150ns, A=1, B=1, C=1 , D=1 , Out=1
Simulation complete via $finish(1) at time 160 NS + 0
/kmap tb.v:41 #`INTERVAL $finish;
```

Your waveform :

 

Explanation of your waveform :

Temp[0] is used to store B', Temp[1] is used to store D', Temp[2] is used to store (A+D)', Temp[3] is used to store C', Temp[4] is used to store (C'+B')', Temp[5] is used to store (D'+(C'+B')')', Temp[6] is used to store (B'+(A+D')')', Temp[7] is used to XOR [5] and [6]. Finally, two [7] values are XORed and used as a NOT operation. Removing the outermost NOT gives the final answer.


It can be seen that at the first time point, since ABCD are all 0, temp[0][1][3] are all 1. Temp[2] is $(0+1)' = 0$, temp[6] is $(1+0)' = 0$. By analogy, using the initial values, the final answer can be obtained.

Superlint screenshot and coverage

The screenshot shows the Cadence Superlint tool interface. The main window displays a violation message: "VHDL reserved word 'Out' used as an identifier or label". The violation is categorized as "FILEFORMAT (1)" and "Tag: IDN_NP_SVICY (1)". The code snippet on the right shows a VHDL module named "kmap" with inputs A, B, C, D and output Out. The code includes a "temp" variable and a "nor" function. The console at the bottom shows the execution of the "check_superlint -extract" command, indicating that 8 structural checks and 1 basic lint check were extracted.

Coverage = 1

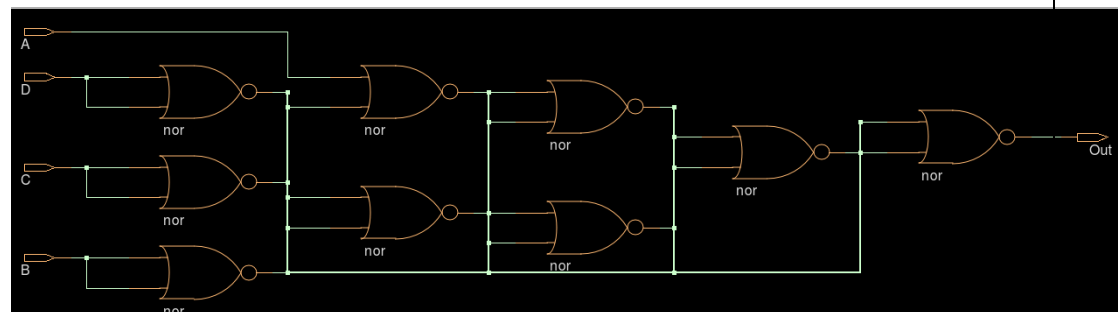- 8) snapshot the schematic view of your design via *nSchema* (Hint : the command is **\$Debussy**)




Prob B: hieratical coding

- 1) An adder is a digital circuit that performs addition of number. Please design a full adder in gate level.
- 2) Draw a full adder in **gate level**.

Inputs			Outputs	
A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

FullAdder

 - 3) Design a full adder in **Structural coding** (The module name should be **FullAdder**. And the file you include should be **FullAdder.v**)
- 4) You only need to upload your v-code to moodle, **do not** paste your code here.
- 5) Design a 6-bit add/sub ripple carry adder in **hierarchical coding**.



Signal	Type	Bits	Description
A	Input	6	First operand
B	Input	6	Second operand


addsub	Input	1	If addsub is 0, operator is addition. If addsub is 1, operator is subtraction.
S	Output	6	Result after calculating
Cout	Output	1	Carry bit
ov_flag	Output	1	If result overflows, ov_flag pull to 1. Otherwise, ov_flag is 0.

- 6) Your design should be named as **ripple_adder.v** and module names in the file should be the same as file name (**ripple_adder**).
- 7) Simulate your design in 2) with the following test pattern in sample testbench.
(Hint: The command for compiling is **%ncverilog ripple_adder.v**)
(Hint: The command for simulation is **%ncverilog ripple_adder_tb.v**
ripple_adder.v +define+FSDB +access+r)
- I. A = 31 ; B = 12 ; addsub = 0;
 - II. A = 7 ; B = -5; addsub = 0;
 - III. A = -10 ; B = 13 ; addsub = 0;
 - IV. A = -31; B = -24 ; addsub = 0;
 - V. A = -31; B = -24 ; addsub = 1;
 - VI. A = -28; B = 10 ; addsub = 1;
 - VII. A = 8; B = 31; addsub = 1;
 - VIII. A = 20 ; B = 7 ; addsub = 1;
 - IX. A = 22 ; B = -25 ; addsub = 1;
- 8) Verify your design by comparing the simulation results with the results you predicted. If the results are not the same, please go back to 2) and revise your code. If the simulation results are correct, please snapshot the simulation result on the terminal and the waveform you dumped and explain your waveform.
(Hint : The command to open nWave is **%nWave &**)
In addition, you should check your coding style, there are no error messages and over 90% coverage with Superlint. Snapshot the result and *calculate Superlint coverage*. (Hint: The command to open Superlint is **%jg -superlint superlint.tcl**)

Your simulation result on the terminal.

```
*Verdi* : End of traversing.
      0ns, A=011111, B=001100, addsub=0, S=43, Cout=0, ov_flag=1
     10ns, A=000111, B=111011, addsub=0, S= 2, Cout=1, ov_flag=0
     20ns, A=110110, B=001101, addsub=0, S= 3, Cout=1, ov_flag=0
     30ns, A=100001, B=101000, addsub=0, S= 9, Cout=1, ov_flag=1
     40ns, A=100001, B=101000, addsub=1, S=57, Cout=0, ov_flag=0
     50ns, A=100100, B=001010, addsub=1, S=26, Cout=1, ov_flag=1
     60ns, A=001000, B=011111, addsub=1, S=41, Cout=0, ov_flag=0
     70ns, A=010100, B=000111, addsub=1, S=13, Cout=1, ov_flag=0
     80ns, A=010110, B=100111, addsub=1, S=47, Cout=0, ov_flag=1
Simulation complete via $finish(1) at time 90 NS + 0
```


Your waveform :

 

Explanation of your waveform :

When between 0 and 1, since addsub = 0, addition is performed. The value of B is placed into B_temp without any operation. Then, FullAdders are used for addition. Finally, ov_flag is calculated by XORing the Cout of the last two bits to determine if there is an overflow. When between 4 and 5, since addsub = 1, subtraction is performed. The value of B is converted to a negative number using 1's complement and stored in B_temp for calculation. Also, Cin = 1 in the first FA, which can be like 2's complement form to get the correct answer. The overflow judgment method is the same as above, and so on.

Superlint screenshot and coverage

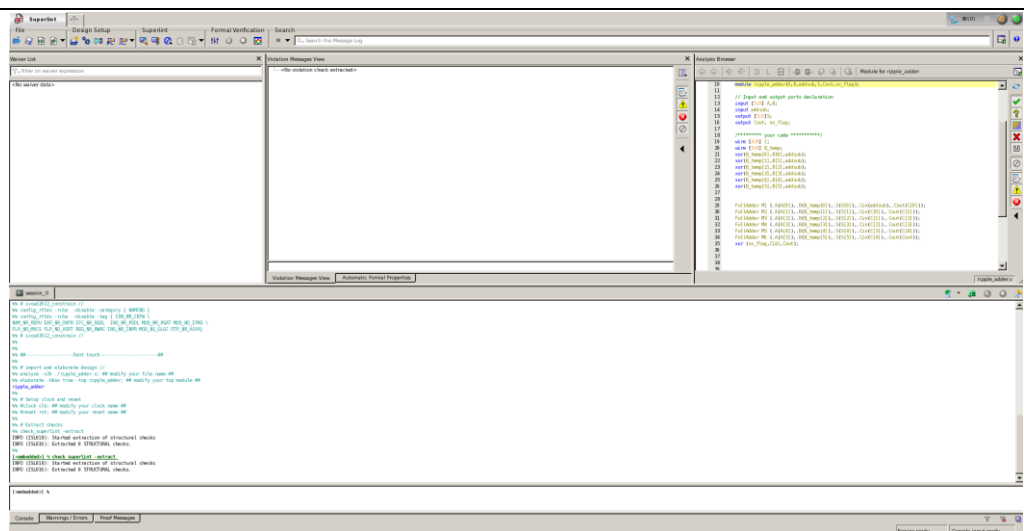


Coverage = 1

Prob C: Application

- 1) Design a 3x3 bits multiplier using RCAs of Prob B, also designed at gate level rather than behavior level. (The module name should be **multi**. And the file you include should be **multi.v**)
 - 2) Draw your hierarchical structure.
 - 3) You only need to upload your v-code to moodle, do not paste your code here.
 - 4) Simulate your design in 2) with the testbench which includes all case of input. (Hint: The command for compiling is **%ncverilog multi.v**
(Hint: The command for simulation is **%ncverilog multi_tb.v multi.v +define+FSDB +access+r**)
 - 9) Verify your design by comparing the simulation results with the results you predicted. If the results are not the same, please go back to 2) and revise your code. If the simulation results are correct, please snapshot the simulation result on the terminal and the waveform you dumped and explain your waveform. (Hint : The command to open nWave is **%nWave &**)
- In addition, you should check your coding style, there are no error messages and over 90% coverage with Superlint. Snapshot the result and *calculate Superlint coverage*. (Hint: The command to open Superlint is **%jg -superlint superlint.tcl**)

Draw your hierarchical structure.

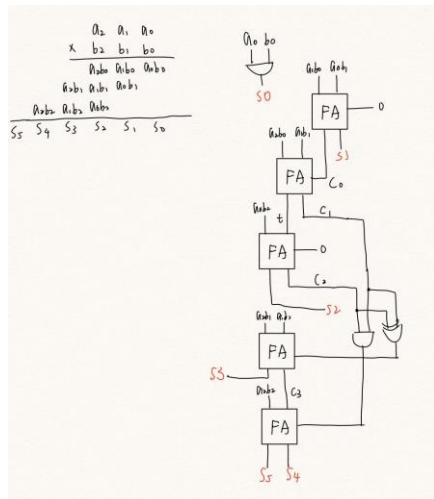


Your simulation result on the terminal.

```

70ns, A=0, B=6, S in decimal= 0, S in binary=000000
80ns, A=0, B=7, S in decimal= 0, S in binary=000000
90ns, A=1, B=0, S in decimal= 0, S in binary=000000
100ns, A=1, B=1, S in decimal= 1, S in binary=000001
110ns, A=1, B=2, S in decimal= 2, S in binary=000010
120ns, A=1, B=3, S in decimal= 3, S in binary=000011
130ns, A=1, B=4, S in decimal= 4, S in binary=000100
140ns, A=1, B=5, S in decimal= 5, S in binary=000101
150ns, A=1, B=6, S in decimal= 6, S in binary=000110
160ns, A=1, B=7, S in decimal= 7, S in binary=000111
170ns, A=2, B=0, S in decimal= 0, S in binary=000000
180ns, A=2, B=1, S in decimal= 2, S in binary=000010
190ns, A=2, B=2, S in decimal= 4, S in binary=000100
200ns, A=2, B=3, S in decimal= 6, S in binary=000110
210ns, A=2, B=4, S in decimal= 8, S in binary=001000
220ns, A=2, B=5, S in decimal=10, S in binary=001010
230ns, A=2, B=6, S in decimal=12, S in binary=001100
240ns, A=2, B=7, S in decimal=14, S in binary=001110
250ns, A=3, B=0, S in decimal= 0, S in binary=000000
260ns, A=3, B=1, S in decimal= 3, S in binary=000011
270ns, A=3, B=2, S in decimal= 6, S in binary=000110
280ns, A=3, B=3, S in decimal= 9, S in binary=001001
290ns, A=3, B=4, S in decimal=12, S in binary=001100
300ns, A=3, B=5, S in decimal=15, S in binary=001111
310ns, A=3, B=6, S in decimal=18, S in binary=010010
320ns, A=3, B=7, S in decimal=21, S in binary=010101
330ns, A=4, B=0, S in decimal= 0, S in binary=000000
340ns, A=4, B=1, S in decimal= 4, S in binary=000100
350ns, A=4, B=2, S in decimal= 8, S in binary=001000
360ns, A=4, B=3, S in decimal=12, S in binary=001100
370ns, A=4, B=4, S in decimal=16, S in binary=010000
380ns, A=4, B=5, S in decimal=20, S in binary=010100
390ns, A=4, B=6, S in decimal=24, S in binary=011000
400ns, A=4, B=7, S in decimal=28, S in binary=011100
410ns, A=5, B=0, S in decimal= 0, S in binary=000000
420ns, A=5, B=1, S in decimal= 5, S in binary=000101
430ns, A=5, B=2, S in decimal=10, S in binary=001010
440ns, A=5, B=3, S in decimal=15, S in binary=001111
450ns, A=5, B=4, S in decimal=20, S in binary=010100
460ns, A=5, B=5, S in decimal=25, S in binary=011001
470ns, A=5, B=6, S in decimal=30, S in binary=011110
480ns, A=5, B=7, S in decimal=35, S in binary=100011
490ns, A=6, B=0, S in decimal= 0, S in binary=000000
500ns, A=6, B=1, S in decimal= 6, S in binary=000110
510ns, A=6, B=2, S in decimal=12, S in binary=001100
520ns, A=6, B=3, S in decimal=18, S in binary=010010
530ns, A=6, B=4, S in decimal=24, S in binary=011000
540ns, A=6, B=5, S in decimal=30, S in binary=011110
550ns, A=6, B=6, S in decimal=36, S in binary=100100
560ns, A=6, B=7, S in decimal=42, S in binary=101010
570ns, A=7, B=0, S in decimal= 0, S in binary=000000
580ns, A=7, B=1, S in decimal= 7, S in binary=000111
590ns, A=7, B=2, S in decimal=14, S in binary=001110
600ns, A=7, B=3, S in decimal=21, S in binary=010101
610ns, A=7, B=4, S in decimal=28, S in binary=011100
620ns, A=7, B=5, S in decimal=35, S in binary=100011
630ns, A=7, B=6, S in decimal=42, S in binary=101010
640ns, A=7, B=7, S in decimal=49, S in binary=110001

```

Your waveform :

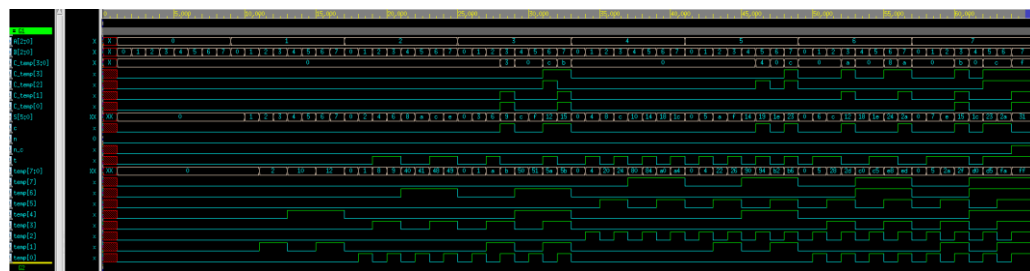


Explanation of your waveform :

It can be seen from the hierarchical structure above what values are stored in C_temp and temp, respectively. It can be seen that at 36, *which is 011110*, there is a carry when operating S[2], so there will also be a carry when operating S[3]. Among them, c and n_c are used when operating S[2] because the three temps are added together. Therefore, it is possible that C_temp[1]

and [2] are both 1, which will directly enter the next two bits. Therefore, $n_c = \text{and}(\text{temp}[1], \text{temp}[2])$ is used as the Cin of S[4], and when there is only one 1, it can directly enter S[3] as Cin. When both are = 0, there is no need to carry. Therefore, $c = \text{xor}(c_temp[1], c_temp[2])$. It can be seen that at this time $c_temp[1] = 0$ and $c_temp[2] = 1$, which means that only one bit will be carried. Therefore, $c = 1$ and $n_c = 0$, which means that the cin of $s[3] = 1$. Then the general FA is done later, and so on.

Superlint screenshot and coverage

 

Coverage = 1

Appendix A : Commands we will use to check your homework

Problem		Command
ProbA	Compile	% ncverilog kmap.v
	Simulate	% ncverilog kmap_tb.v kmap.v +access+r +define+FSDB
ProbB	Compile	% ncverilog ripple_adder.v
	Simulate	% ncverilog ripple_adder_tb.v ripple_adder.v +access+r +define+FSDB
ProbC	Compile	% ncverilog multi.v
	Simulate	% ncverilog multi_tb. sv multi.v +access+r +define+FSDB