

VLSI Circuit Design

Lab 1

Yu-Chi Chu

Problem 1 - Pass Transistor and 2-1 MUX

(a) schematic

 


Fig 1_1 NMOS pass transistor

 


Fig 1_2 PMOS pass transistor

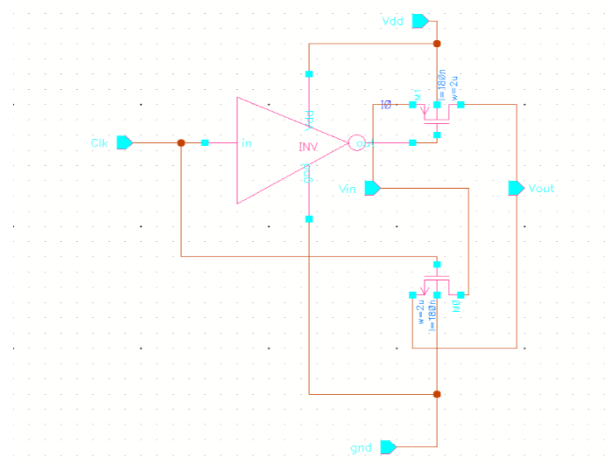


Fig 1_3 Transmission gate

(b) waveform



Fig 1_4 NMOS pass transistor



Fig 1_5 PMOS pass transistor

 


Fig 1_6 Transmission gate

(c) Explain

- **NMOS Pass Transistor:** When $\text{Clk}=1$ (clock high), the NMOS transistor is ON (conducting), and V_o (output voltage) is equal to V_{in} (input voltage). However, due to the NMOS transistor's characteristic of passing a "strong 0" but a "degraded 1," the output voltage V_o will not reach V_{dd} (supply voltage) completely. When $\text{Clk}=0$ (clock low), the NMOS transistor is OFF (non-conducting), and V_o is equal to ground ($\text{gnd}=0$).
- **PMOS Pass Transistor:** When $\text{Clk}=0$ (clock low), the PMOS transistor is ON (conducting), and V_o (output voltage) is equal to V_{in} (input voltage). However, due to the PMOS transistor's characteristic of passing a "strong 1" but a "degraded 0," the output voltage V_o will not reach ground ($\text{gnd}=0$) completely. When $\text{Clk}=1$ (clock high), the PMOS transistor is OFF (non-conducting), and V_o is equal to V_{dd} (supply voltage).
- **Transmission Gate:** When $\text{Clk}=1$ (clock high), both the NMOS and PMOS transistors in the transmission gate are ON (conducting), and V_o (output voltage) is equal to V_{in} (input voltage). Because the transmission gate combines the advantages of both NMOS and PMOS transistors (passing both "strong 0" and "strong 1"), the output voltage V_o can reach both V_{dd} (supply voltage) and ground ($\text{gnd}=0$) completely. When $\text{Clk}=0$ (clock low), both transistors are OFF (non-conducting), and V_o is equal to 0.

Because the transmission gate possesses the characteristics of passing both "strong 0" and "strong 1," it provides better performance compared to using a single MOS transistor and is therefore more widely used.

(d) schematic

 


Fig 1_7 Transmission gate multiplexer

(e) waveform

 


Fig 1_8 Transmission gate multiplexer

(f) layout

 


Fig 1_9 Transmission gate multiplexer layout

(g)PEX waveform


 


Fig 1_12 Transmission gate multiplexer PEX waveform

Problem 2 - D Latch and D Flip-Flop

(a) schematic

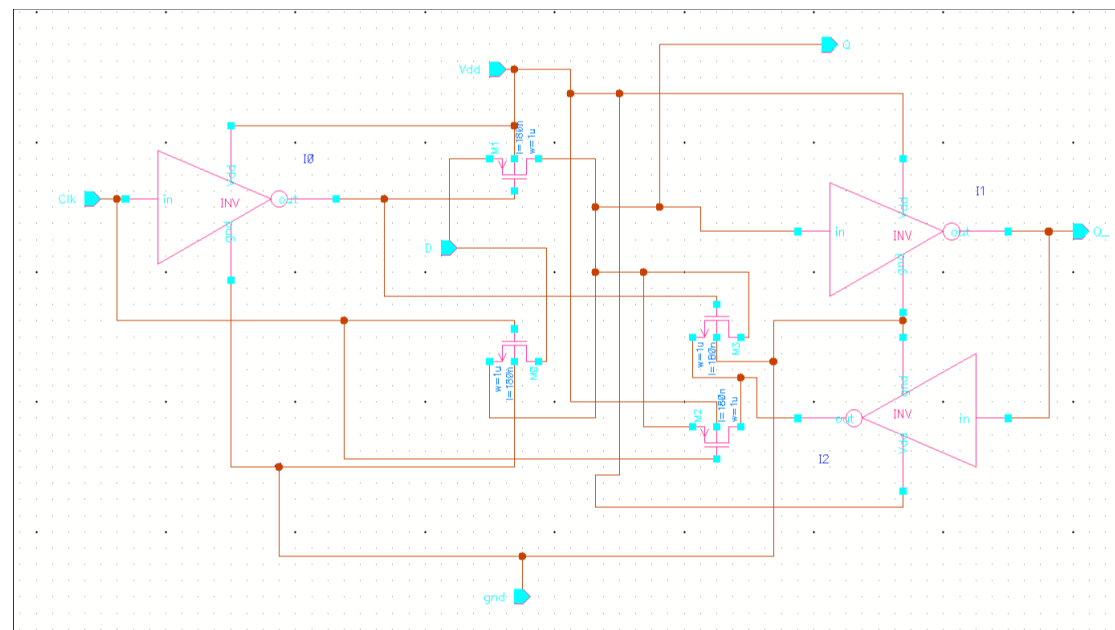

 


Fig 2_2 D Flip-Flop

(b) waveform

 


Fig 2_3 D latch

 


Fig 2_4 D Flip-Flop

(c) layout

 


Fig 2_5 D latch layout

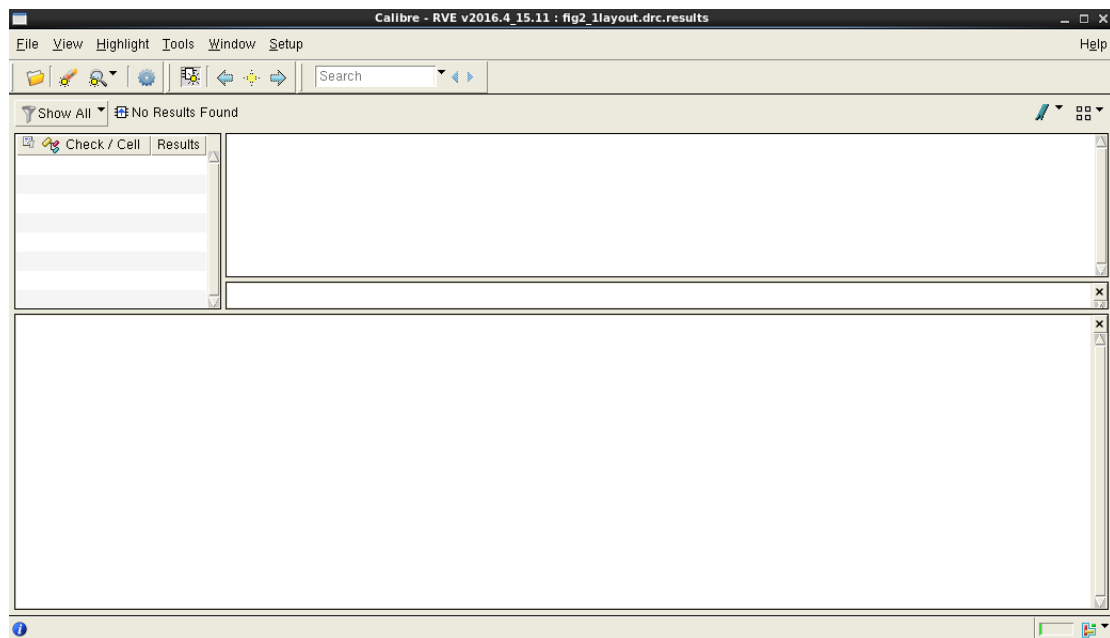


Fig 2_6 D latch DRC

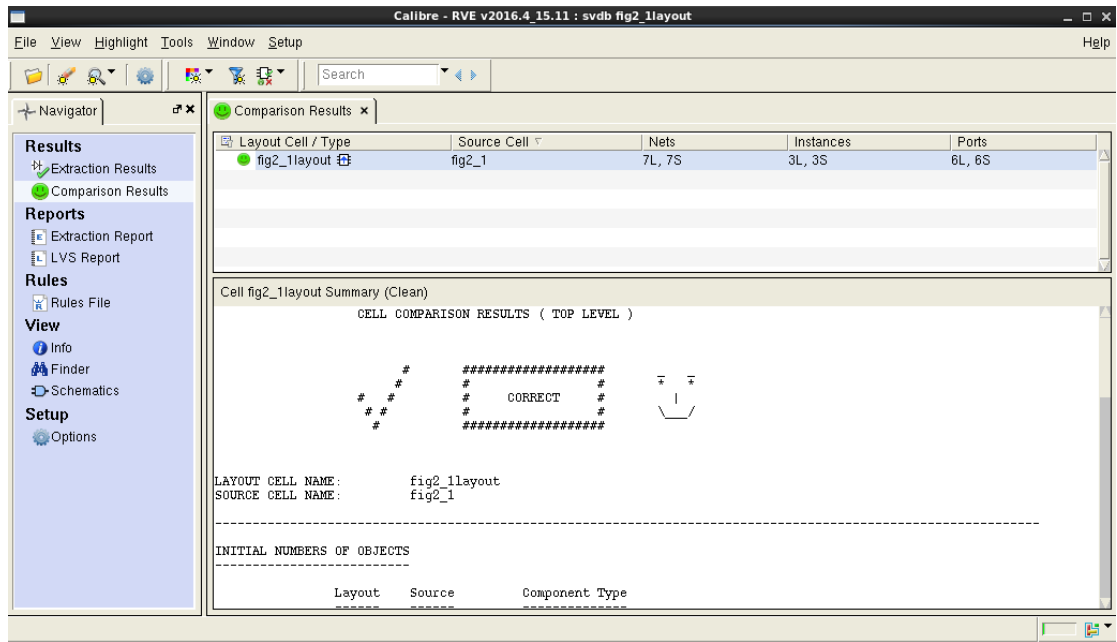


Fig 2_7 D latch LVS

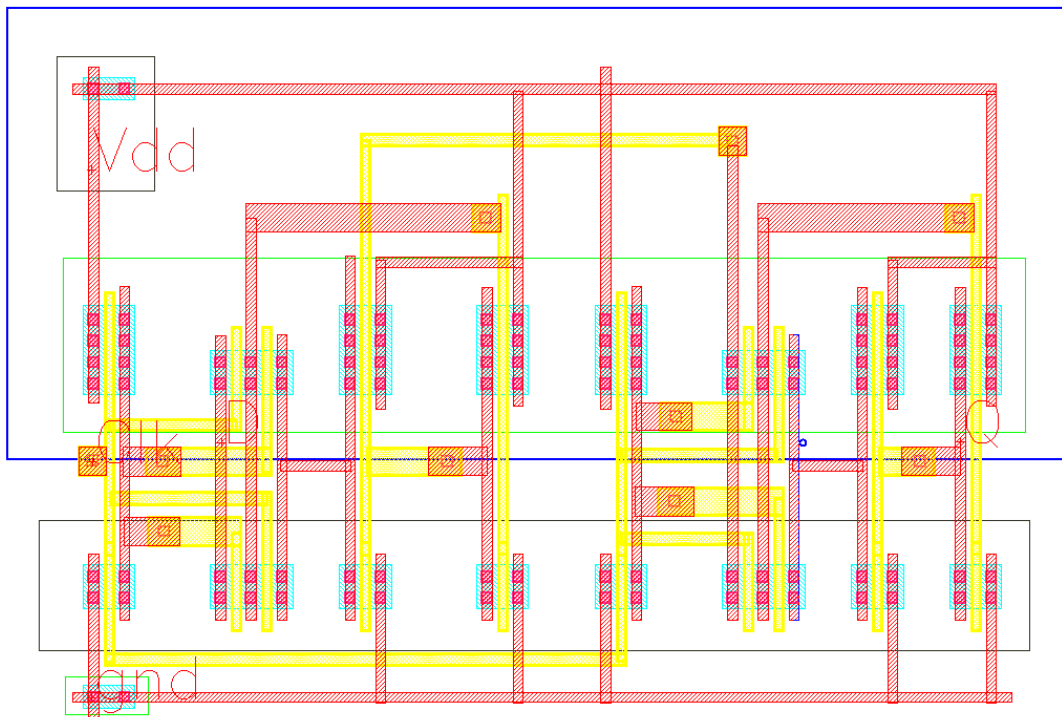


Fig 2_8 D Flip-Flop layout



(d) PEX waveform

 


Fig 2_11 D latch PEX waveform

 


Fig 2_12 D Flip-Flop PEX waveform

Problem 3 – Combinational logic design

(a) schematic

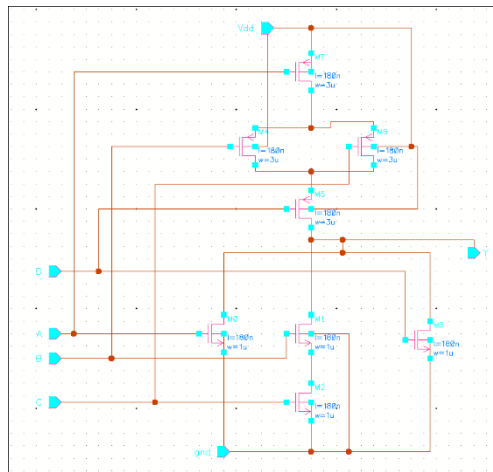


Fig 3_1 Function 1

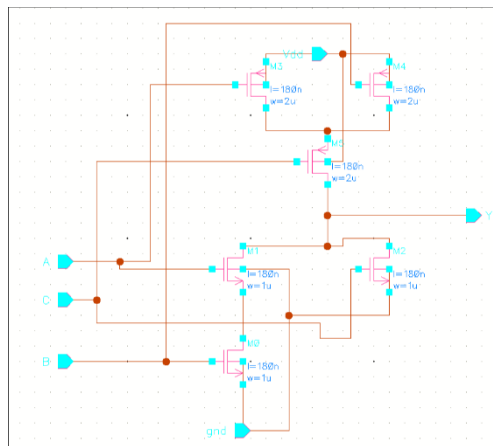


Fig 3_2 Function 2

(b) waveform

 


Fig 3_3 Function 1

 


Fig 3_4 *Function 2*

(c) layout

 


Fig 3_5 *Function 1 layout*

 


Fig 3_8 *Function 2* layout

 


Fig 3_9 *Function 2* DRC



Fig 3_12 *Function 2* PEX waveform